
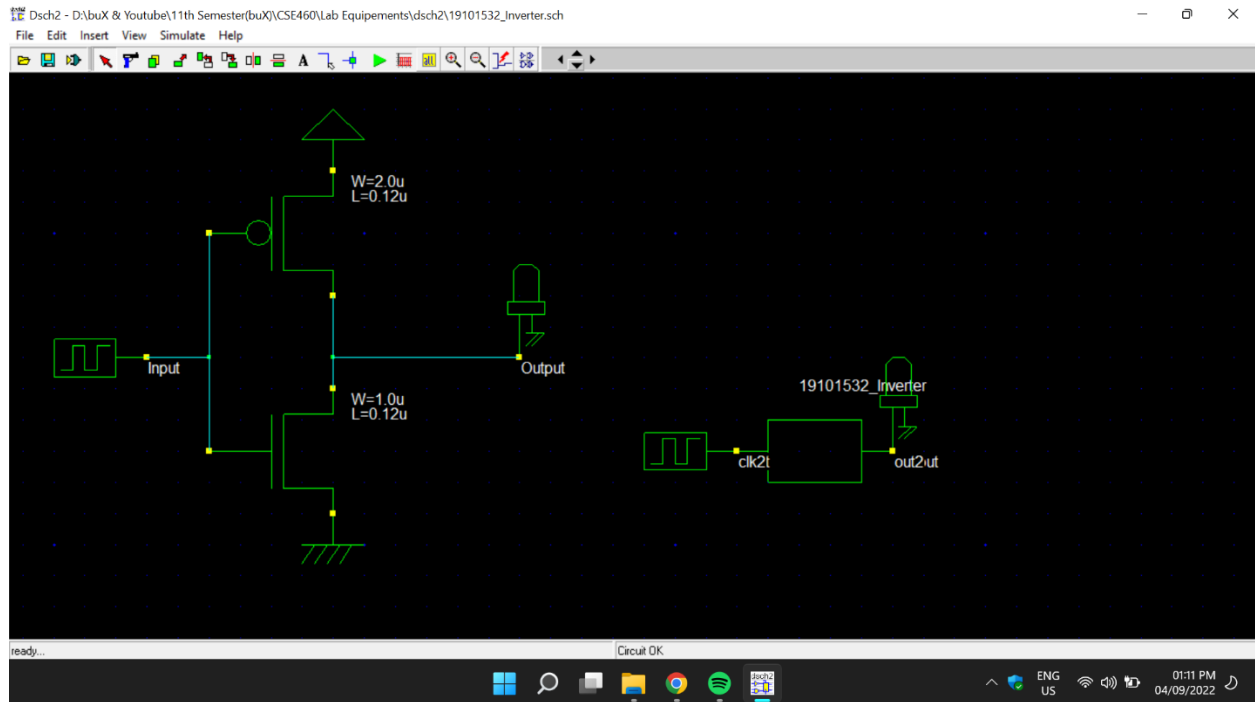


Assignment 3


Inverter:

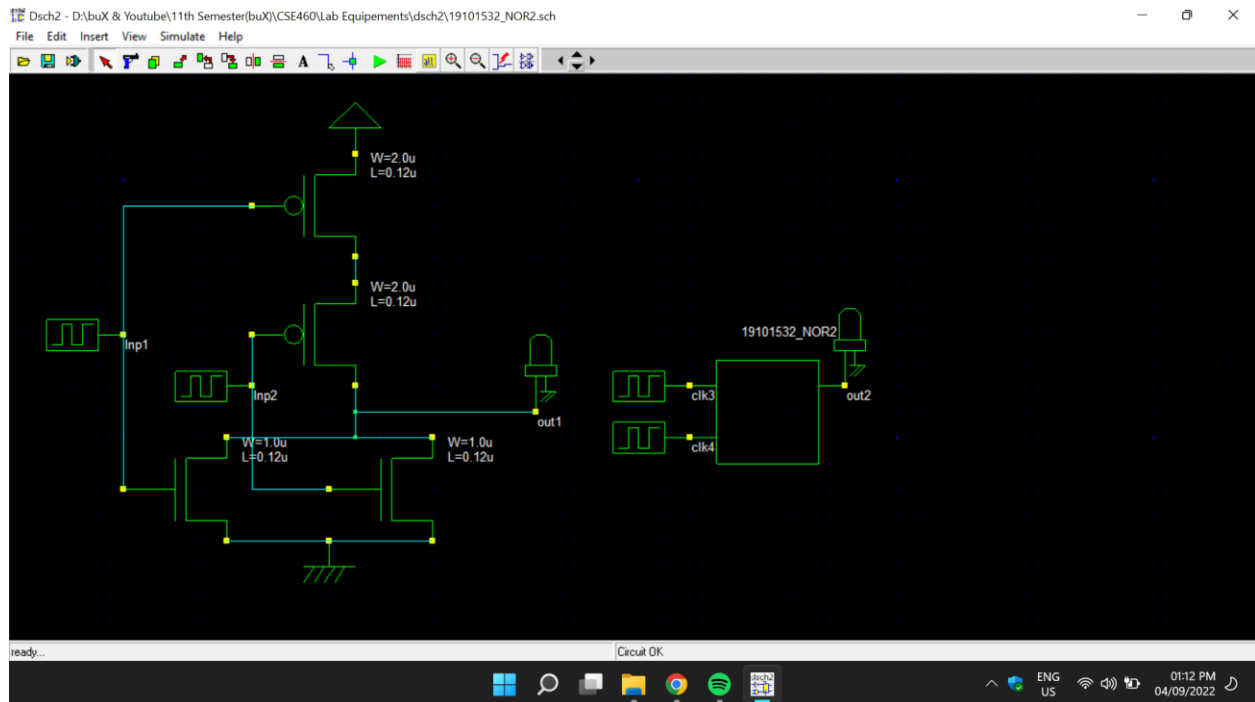


NOR2:




NAND2:

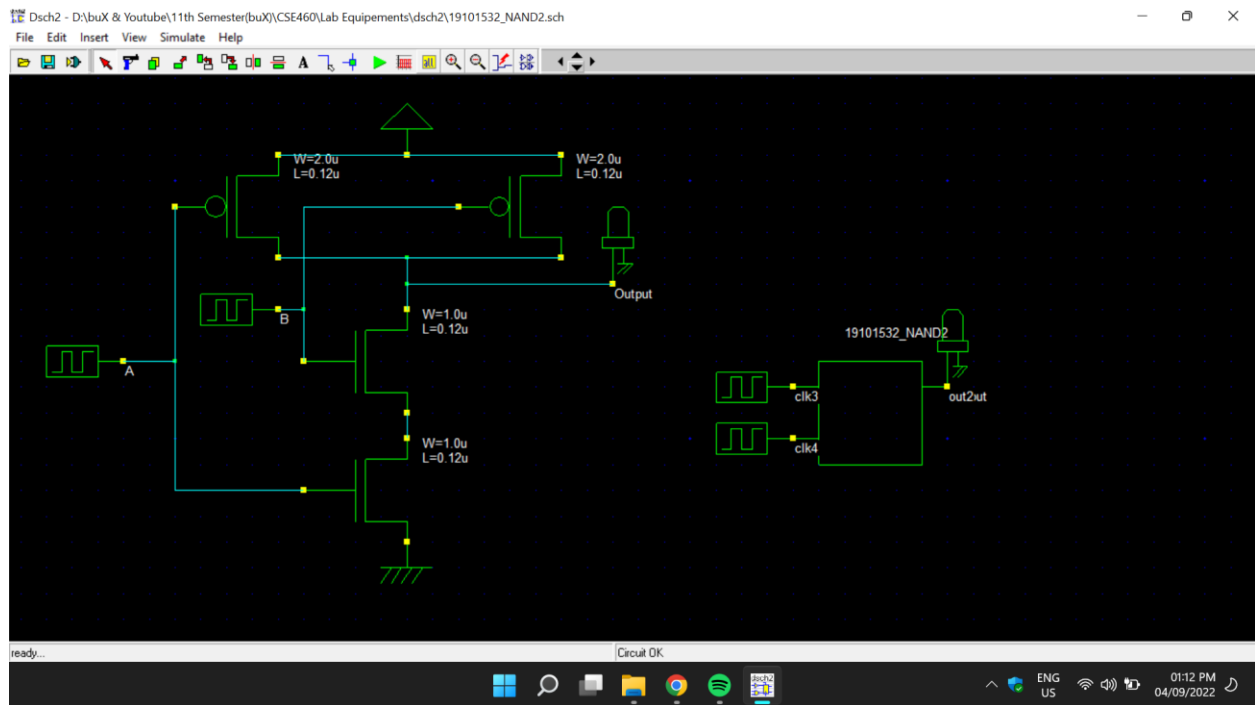

$\sim((A+B)(C+D))$:

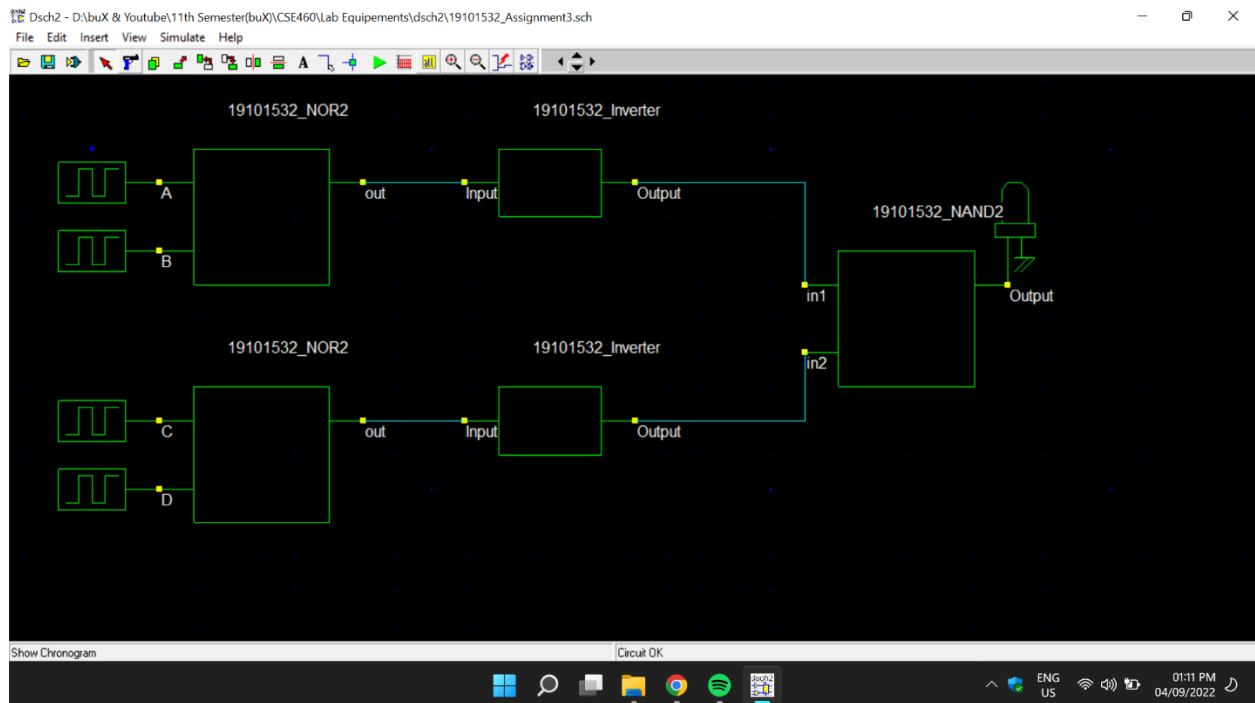


Timing Diagram:

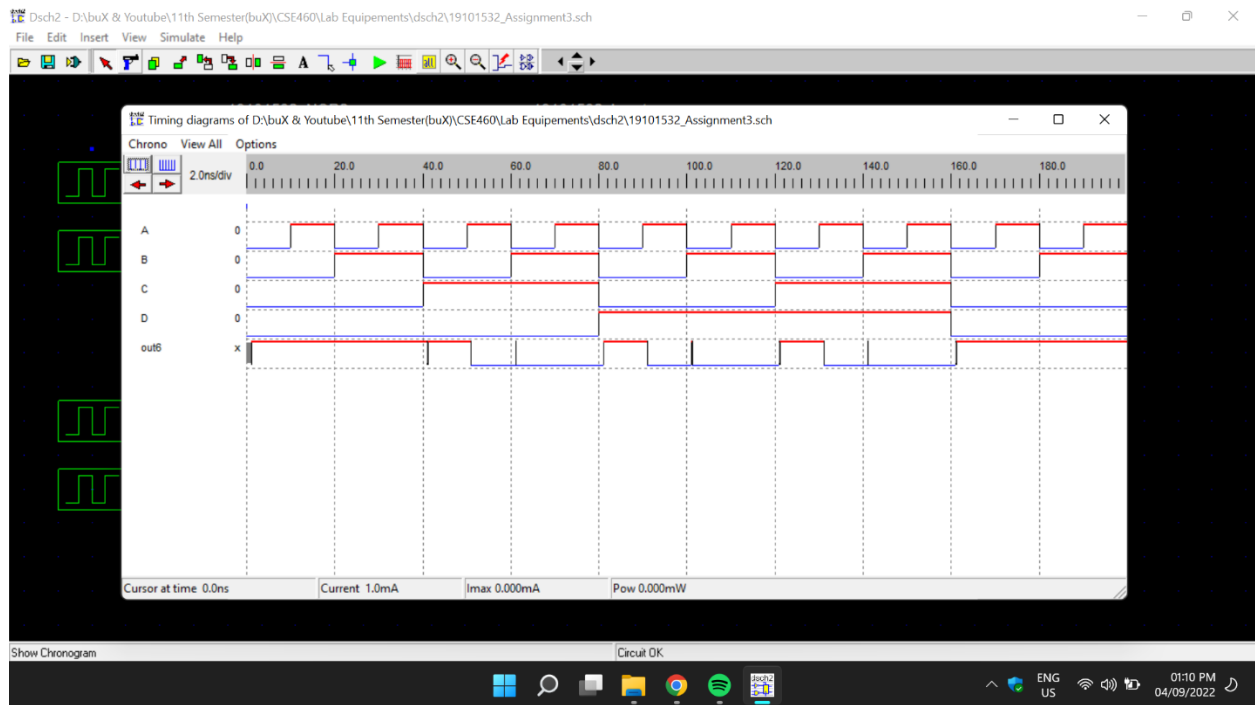

Assignment 4

Layout Design:

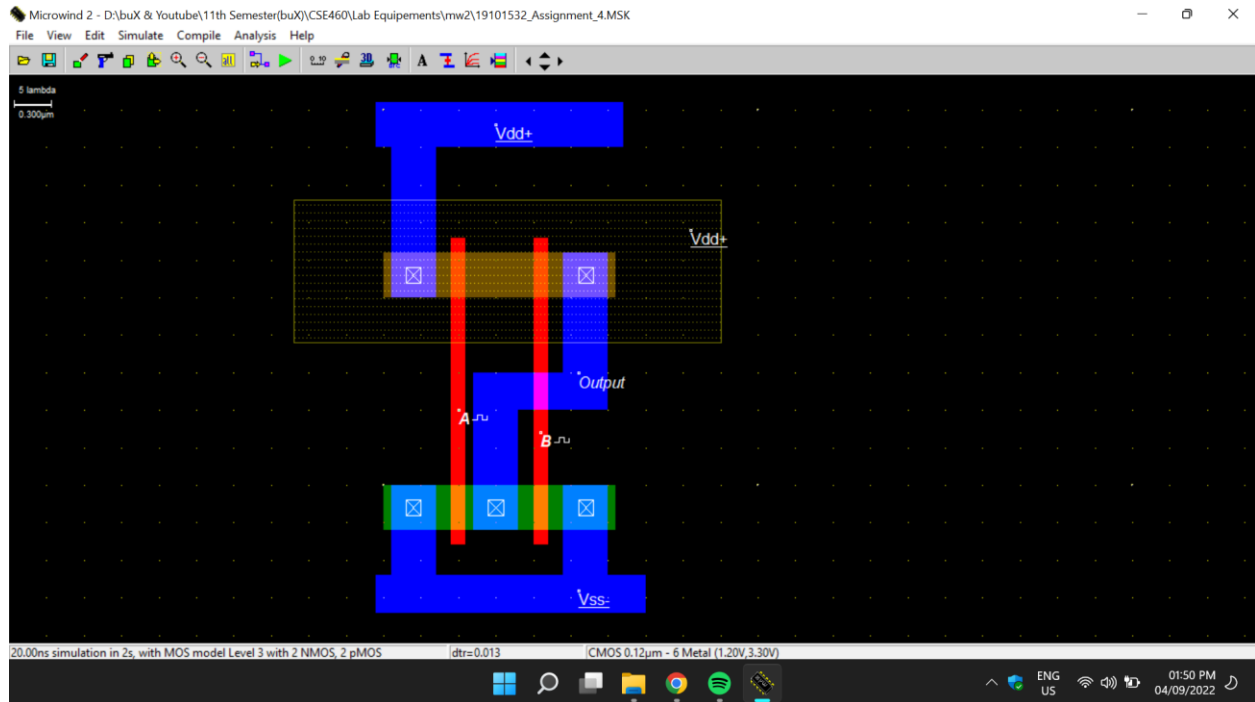

Waveform:

